


CSCI 160 SPRING 2025
MIDTERM EXAM 3
SAMPLE

Name:										
EMPLID:										

◆ Part I ◆

1. Which of the following best describes a combinational circuit?
 - (a) It stores previous inputs to determine outputs
 - (b) It uses feedback loops and memory elements
 - (c) Its outputs depend only on the current combination of inputs
 - (d) Its behavior is determined by a sequence of states over time
2. What is the key difference between combinational and sequential circuits?
 - (a) Combinational circuits require memory elements
 - (b) Sequential circuits do not use Boolean functions
 - (c) Combinational circuits depend on past inputs
 - (d) Sequential circuits have outputs based on both current and past inputs
3. What additional component do sequential circuits have that combinational circuits do not?
 - (a) Input terminals
 - (b) Storage elements
 - (c) Boolean functions
 - (d) Output gates
4. How is the behavior of a sequential circuit best specified?
 - (a) With a truth table
 - (b) Using only Boolean expressions
 - (c) By a time sequence of inputs and internal states
 - (d) Through output waveforms only
5. Which statement is TRUE about combinational circuits?
 - (a) They can remember past inputs
 - (b) They consist of logic gates and storage elements
 - (c) Their outputs change based on internal states
 - (d) Their outputs are determined solely by present inputs

◆ Part II ◆

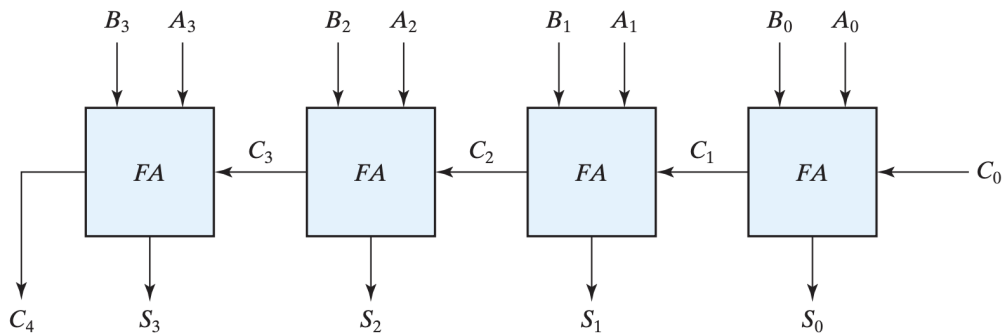

1. Consider the four-bit adder given above. Calculate the sum for each binary arithmetic equation and label the coefficients correctly.

(a) What is the sum of $1010 + 1100$?

(b) What are the values of A_0 to A_3 ?

(c) What are the values of B_0 to B_3 ?

(d) What are the values of C_0 to C_4 ?

(e) What are the values of S_0 to S_3 ?

Name:								
EMPLID:								

◆ Part III ◆

1. Draw the truth table for a 3-to-8-line decoder. Your inputs should be sorted in ascending order.

--

2. Draw the truth table for an octal-to-binary encoder, as presented in the textbook. Your inputs should be sorted in ascending order.

--

3. Given the circuit diagram for a two-to-one-line multiplexer, choose the correct output for Y when $S = 0$ and $S = 1$.

--

4. What is the maximum number of output lines for an n -to- m -line decoder, where $n = 5$?

--

5. How many input lines are there for an n -to- m -line decoder, where $n = 5$?

--

6. Given a four-variable K-map, write a minimized sum-of-products expression.

--

7. Given a formula in standard form, give the total number of gates required to implement the equivalent two-level digital logic circuit.

--

8. Half Adder; draw truth table and digital logic circuit diagram

--

9. 4-bit binary code with unused bit combinations x,y,z; in converting this code to another, what would be the don't care conditions (design question)

--